

# AN839: Novel Current-Sense Measurement with Automatic Offset Correction


---

Pairing a simple circuit using nanopower analog op amps with a microcontroller can monitor single battery cells and solar harvesters. Pairing up a 0.65 V/1  $\mu$ A nanopower op amp with the low-power Cypress PSoC3 microcontroller and some simple external circuitry can yield a very low current measurement system, suitable for monitoring miniature power harvesting solar cells or a single-cell battery. The circuit operates on a few microamps at 1.8 V; optionally, the whole circuit can be self-powered from the source being measured. The op amps operate from voltages as low as 0.65 V and are connected directly to the cells; the PSoC3 microcontroller utilizes an internal boost regulator which operates from sources as low as 0.5 V.

## KEY POINTS

- Operates at 0.8 V
- Runs on a few microamps and is accurate to  $\pm 1 \mu$ A

## 1. Introduction

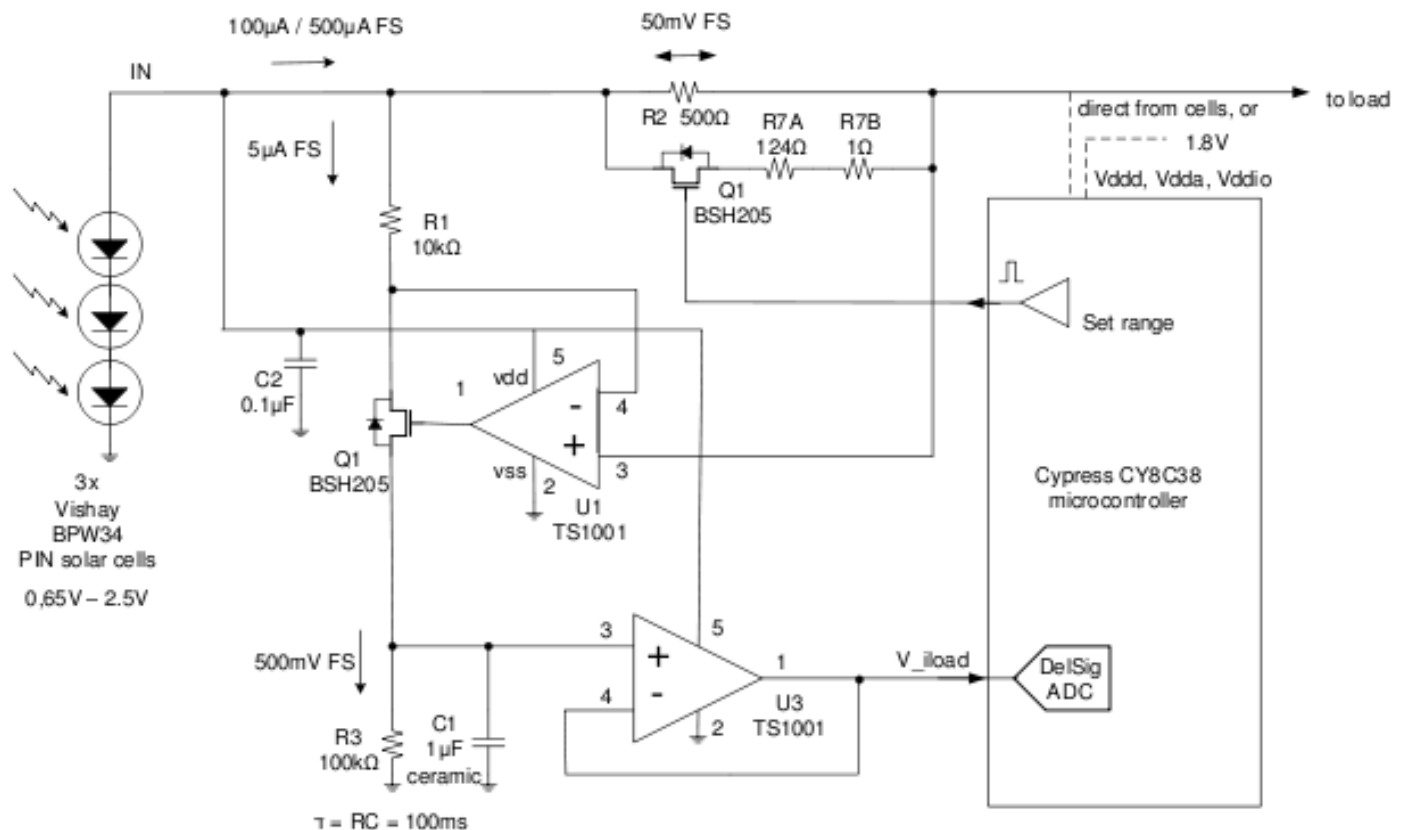

**Figure 1.1. Current-Sense Amplifier with Input Offset Voltage Correction**

The current sense amplifier is shown above. The analog portion of the circuit operates from as low as 0.65 V and draws 860 nA at no load. The circuit provides a 0-500 mV output for measured currents of 0-100  $\mu$ A, though the scale can be adjusted by changing the values of a few resistors. With its extremely low power, the circuit can simply remain always on, providing a continuously monitored, averaged indication of current. The CY8C38 subsequently reads the value periodically, remaining in sleep mode and consuming less than 8  $\mu$ A.

The analog circuit features the TS1001, a nanopower op amp capable of supply voltage operation to 0.65 V configured to servo P-channel MOSFET Q1 in a current source configuration. The current source, draws current through R1 to compensate for the voltage drop across R2 caused by the current flow from the IN terminal to the load. Resistor R3 converts the current to a voltage and C1 provides filtering. The filtering is critical in allowing the current sense amplifier to continuously provide an averaged current output, enabling the microcontroller to sleep for long periods and save power, waking only periodically to read this mean current level.

Current used by Cypress CY8C38	Current used by the Current Sense Amplifier
8 $\mu$ A (average, polling)	860 nA

The accuracy of the circuit is extremely good and is generally limited only by the accuracy of the resistors used. 1% resistors yielded an error of no more than 1  $\mu$ A.

Op amp input offset voltages need to be considered carefully in this circuit. The TS1001 op amp is specified with  $\pm 3$ mV maximum input offset voltage at 25  $^{\circ}$ C, which corresponds to  $\pm 3$  mA of error. Another consideration is that Q1 exhibits drain-source leakage current of a few 10s of nanoamps at 25  $^{\circ}$ C, but this can approach 1  $\mu$ A over the commercial temperature range. Since the current through Q1 is effectively controlled by the op amp loop; therefore, any drain-source leakage from Q1 appears as a current floor and this generates a corresponding minimum voltage output across R3 below which current cannot be measured until the op amp takes over at higher measured currents. Therefore, normal methods of removing the current sense amplifier offset by subtracting the zero-load voltage at V\_ilo will not work, since the offset voltage due to the op amp's VOS and the current floor from Q1's drain-source leakage cannot be separated.

Therefore, the offset correction scheme utilizing Q1 and R7 is implemented. Amplifier input offset voltage may be calibrated out using the principal of making two measurements of the same parameter at the two gain settings. The offset voltage then can be found as the following:

$$V_{\text{OFFSET}} = V_{\text{ILOAD\_G2}} \times \frac{R_{\text{G1}}}{R_{\text{G1}} - R_{\text{G2}}} - V_{\text{ILOAD\_G1}} \times \frac{R_{\text{G2}}}{R_{\text{G1}} - R_{\text{G2}}}$$

where Vload\_G1 and Vload\_G2 are the measurements made with low range and high range mode, respectively, and where:

$$R_{\text{G1}} = R_2$$

$$R_{\text{G2}} = \frac{R_2 R_7}{R_2 + R_7}$$

In this case, RG1 = 500 and RG2 = 100, effectively providing two scales of 100  $\mu$ A and 500  $\mu$ A full scale, respectively. The CY8C38 Microcontroller Code for Offset-Voltage-Corrected Current-Sense Amplifier follows:

```

/*****
* File Name: main.c
*
* Version: 1.0
*
* Description:
* This is source code for the Current Sense Amplifier
*
*****/
#include
#include


/*****
* Function Name: main
*****/
* Target Device:
* CY8C38 processor
*****/
void main()
{
    int32 ADCResult;
    float Iin;
    float Iin_corrected;
    char OutputString[32];

```

```

float Offset;
int16 Offsetcounter;
Offsetcounter= (int16) 0;
Offset= (float) 0;
LED_P1_2_Write(0xFFu);          // Indicates active mode. Remove LED for Icc.
GAINSWITCH_P1_6_Write(0xFFu); // GAINSWITCH to mode 1
CYGlobalIntEnable;              // global interrupts
//LCD_Start();                  // start components (LCD optional)
isr_Start();
ADC_Start();
SleepTimer_Start();            // sleep timer params set in the GUI
for(;;)
{
    ADC_StartConvert();          // make a conversion and
wait
    while (ADC_IsEndConversion(ADC_RETURN_STATUS) == 0)
    {
        ADCResult = ADC_CountsTo_mVolts(ADC_GetResult32()); // math
        Iin= (float) ADCResult/5; // units microamps
        Iin_corrected= (float) Iin - Offset;
        // Optional LCD display
        /*
        sprintf(OutputString, "%5.3f",Iin_corrected); // 300usecs
        LCD_Position(0,0); // write to L
CD; 700usecs
        LCD_PrintString("I load=");
        LCD_Position(0,8);
        LCD_PrintString(OutputString);
        */
        ADC_StopConvert();
        if (Offsetcounter==32)
        {
            if ((Iin> 50) && (Iin<100))
            {
                GAINSWITCH_P1_6_Write(0x00u); // switch gain to m
ode 2
                CyDelay(50u); // delay
                ADC_StartConvert(); // make a conversio
n and wait
                while (ADC_IsEndConversion(ADC_RETURN_STATUS) == 0)
                {
                    ADCResult = ADC_CountsTo_mVolts(ADC_GetResult32());
                    Offset= (float) ADCResult/5*1.25 - Iin*0.25;
                    // Optional LCD display
                    /*
                    LCD_Position(1,0);
                    LCD_PrintString("Offset= ");
                    sprintf(OutputString, "%5.3f",Offset);
                    LCD_Position(1,8);
                    LCD_PrintString(OutputString);
                    */
                    Offsetcounter= (int16) 0;
                    ADC_StopConvert();
                    GAINSWITCH_P1_6_Write(0xFFu); // switch gain to m
ode 1
                }
            }
            else
            {
                Offsetcounter= (int16) Offsetcounter+1;
                ADC_Sleep();
                LED_P1_2_Write(0x00u); // LED off for sleep mode.
                CyPmSaveClocks(); // sleep mode
                CyPmSleep(PM_SLEEP_TIME_NONE, PM_SLEEP_SRC_CTW);
                CyPmReadStatus(CY_PM_CTW_INT);
                CyPmRestoreClocks(); // wake up
                ADC_Wakeup();
            }
        }
    }
}
/* [] END OF FILE */

```

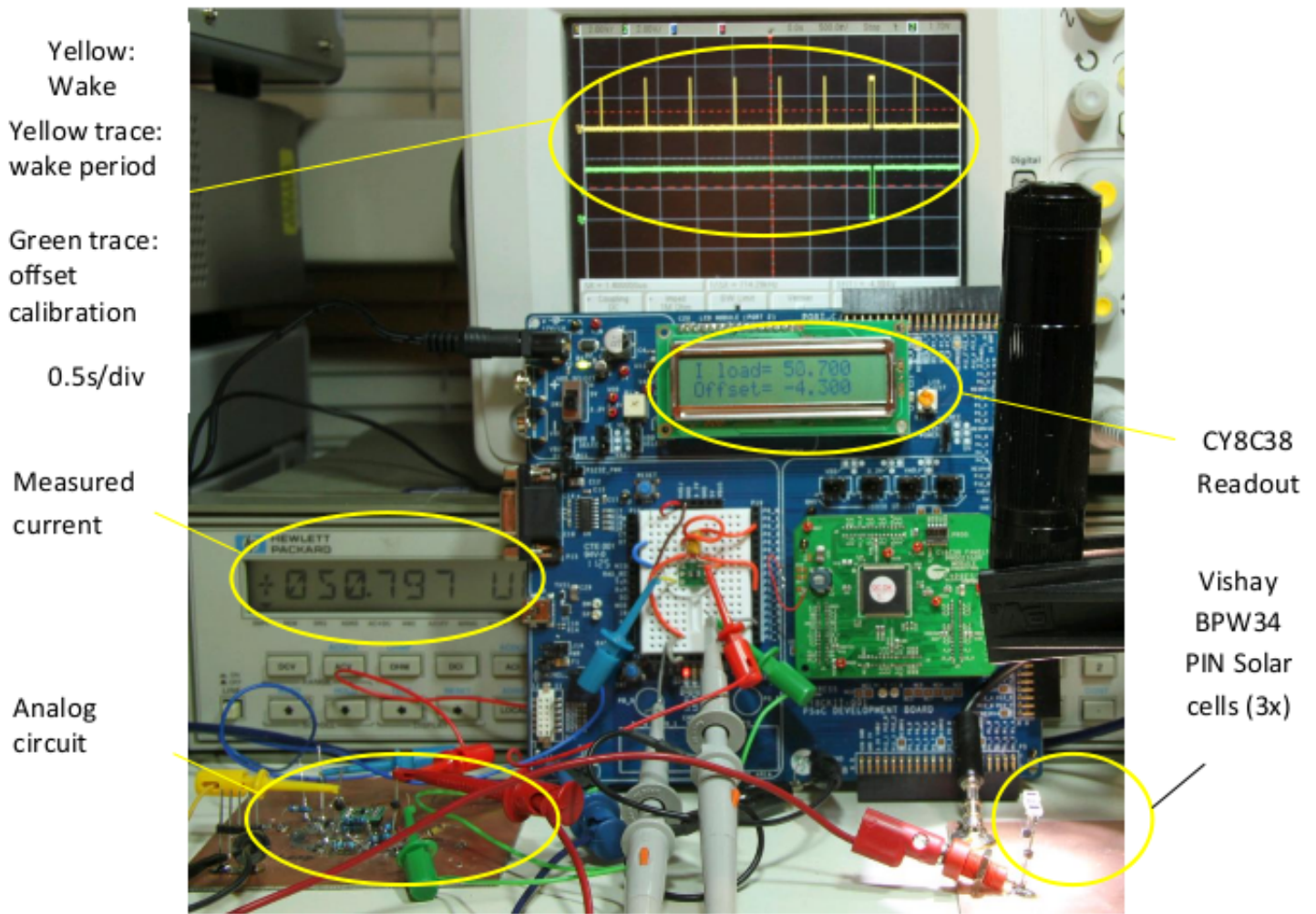

**Figure 1.4. Lab Setup for Offset-Voltage-Corrected Current-Sense Amplifier using the TS1001 and the CY8C38 PSoC3 Microcontroller**

The figure above shows the lab setup. The measured current is shown to match accurately the current estimated by the current sense measurement system. The oscilloscope shows wake periods approximately every 600 msec, with the offset cal period shown by the green trace (the gate voltage of Q1).

See the documentation for the TS1001 Op Amp and CY8C38 PSoC3 Microcontroller. For additional information, contact Silicon Labs.



## ClockBuilder Pro

One-click access to Timing tools, documentation, software, source code libraries & more. Available for Windows and iOS (CBGo only).

[www.silabs.com/CBPro](http://www.silabs.com/CBPro)



**Timing Portfolio**  
[www.silabs.com/timing](http://www.silabs.com/timing)



**SW/HW**  
[www.silabs.com/CBPro](http://www.silabs.com/CBPro)



**Quality**  
[www.silabs.com/quality](http://www.silabs.com/quality)



**Support and Community**  
[community.silabs.com](http://community.silabs.com)

### Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products are not designed or authorized to be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are not designed or authorized for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

### Trademark Information

Silicon Laboratories Inc.®, Silicon Laboratories®, Silicon Labs®, SiLabs® and the Silicon Labs logo®, Bluegiga®, Bluegiga Logo®, Clockbuilder®, CMEMS®, DSPLL®, EFM®, EFM32®, EFR®, Ember®, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZRadio®, EZRadioPRO®, Gecko®, ISOModem®, Precision32®, ProSLIC®, Simplicity Studio®, SiPHY®, Telegesis, the Telegesis Logo®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc.  
400 West Cesar Chavez  
Austin, TX 78701  
USA

<http://www.silabs.com>